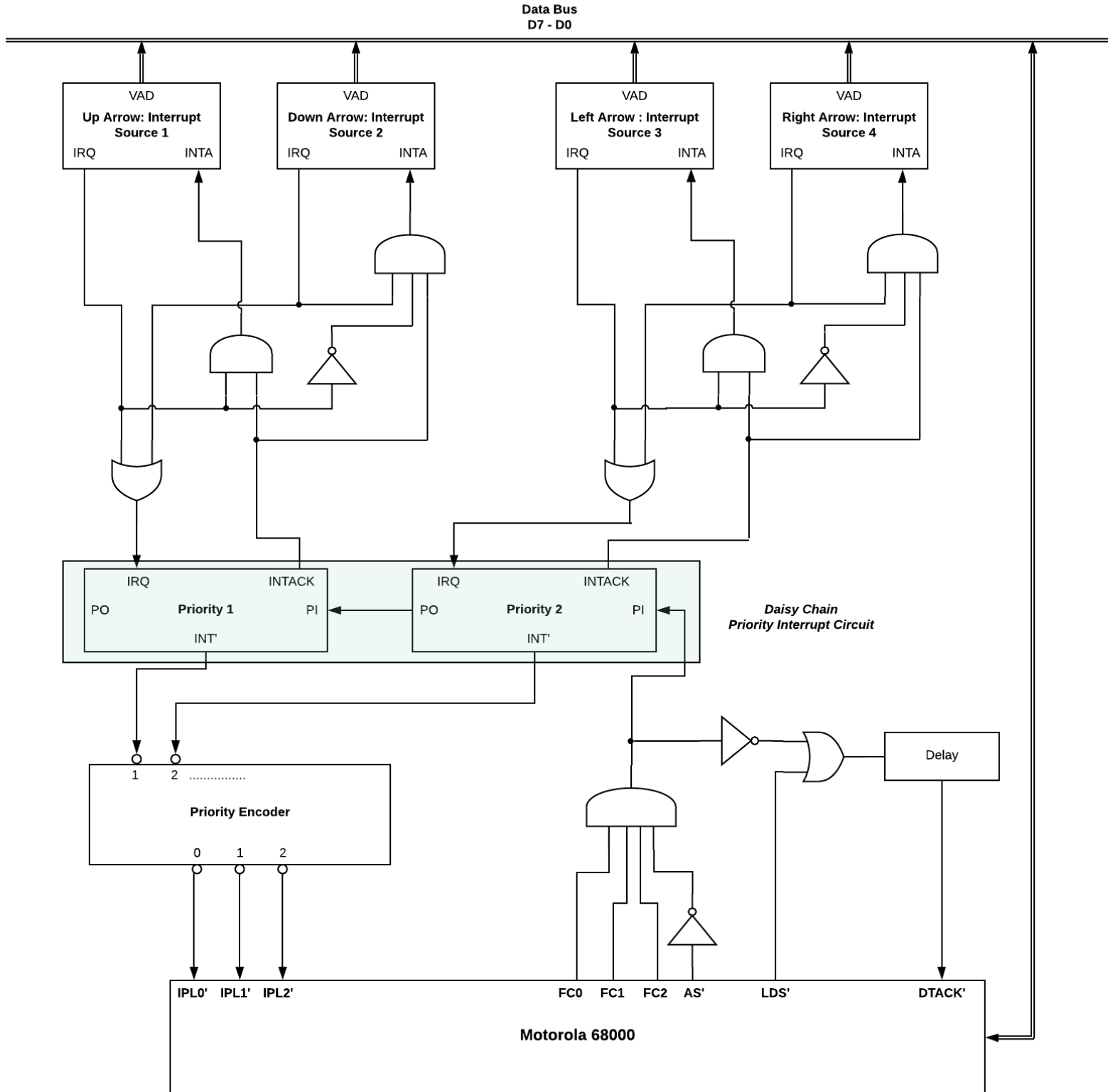


BLG 322E – Computer Architecture

Assignment 3



Left Arrow & Right Arrow Devices

INTA	LEFT_IRQ	RIGHT_IRQ	LEFT_INTA	RIGHT_INTA
0	X	X	0	0
1	0	0	0	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	0

INTA: Interrupt acknowledge signal at priority layer

LEFT_IRQ: Interrupt Request signal of Left Arrow device

RIGHT_IRQ: Interrupt Request signal of Right Arrow device

LEFT_INTA: Interrupt acknowledge signal of Left Arrow Device

RIGHT_INTA: Interrupt acknowledge signal of Right Arrow Device

Using the table above, we come up with two formulas to calculate LEFT_INTA and RIGHT_INTA.

- $LEFT_INTA = INTA \wedge LEFT_IRQ$
- $RIGHT_INTA = INTA \wedge LEFT_IRQ' \wedge RIGHT_IRQ$

Up Arrow & Down Arrow Devices

Same calculations also apply for up arrow and down arrow devices.

- $UP_INTA = INTA \wedge UP_IRQ$
- $DOWN_INTA = INTA \wedge UP_IRQ' \wedge DOWN_IRQ$